



Rev. 1.2E 2022/6/20

Contents

			Page	
1. Pin	Assignment		A-1	
1.1	Pin Assignment		A-1	
2. Con	nection for Standard Use		A-2	
2.1	Connection for standard use		A-2	
2.2	Input fuse	: F11	A-3	
2.3	Input capacitor	: C11	A-3	
2.4	Y capacitors and noise filters	: CY,CX,L11,L12	A-4	
2.5	Output capacitors	: Co,C40	A-4	
2.6	Smoothing capacitor for boost voltage	: Cbc	A-5	
2.7	Capacitor for boost voltage	: C20,C30	A-6	
2.8	Inrush current limiting resistor	: TFR1	A-7	
2.9	Discharging resistor	: R1	A-7	
3. Hol	dup time		A-8	
3.1	Input voltage characteristics of boosted v	oltage	A-8	
3.2	Holdup time		A-8	
4. Ope	eration under low temperature conditio	ns	A-9	
4.1	Ripple voltage of boost voltage		A-9	
5. Par	allel operation		A-11	
5.1	Wiring for parallel operation		A-11	
5.2	Output voltage adjustment in parallel of	peration(CV)	A-12	
5.3	Constant current adjustment in parallel	operation(CC)	A-13	
5.4	N+1 redundant operation		A-14	
5.5	Remote control		A-16	
6. Oth	er functions		A-17	
6.1	Power good		A-17	
6.2	Output Current Monitor		A-18	
7. Mot	unting method		A-19	
7.1	Mounting method		A-19	
8. Boa	rd layout		A-20	
8.1	Consideration for board layout		A-20	
8.2	Reference PCB layout			
9. The	rmal Design		A-25	
9.1	Thermal Design		A-25	
9.2	Examples of Convection cooling			
9.3	3 Examples of Forced air cooling			

Note: Information contained in this document is subject to change without notice for improvement. The materials are intended as a reference design, component values and circuit examples described in this document varies depending on operating conditions and component variations. Please select the components and design under consideration of usage condition etc.

1. Pin Assignment

Applications Manual

TUNS1200

1.1 Pin Assignment



Table 1.1 Pin configuration and function

No	Pin	Function
110.	Connection	1 41101011
1	AC1	AC input
2	AC2	AC input
3	R	External resistor for inrush current protection
4	+BC	+BC output
5	-BC	-BC output
67	+VOUT	+DC output
89	-VOUT	-DC output
10	+S	Remote sensing(-)
1	-S	Remote sensing(+)
(12)	CB	Current balance
13	RC2	Remote ON/OFF ground
14)	PGG	Alarm ground
15	ITRM	Adjustment of output current
16	VTRM	Adjustment of output voltage
1	AUX	Auxiliary output for remote ON/OFF
18	RC1	Remote ON/OFF
19	\overline{PG}	Alarm
-	FG	Mounting hole(FG)

2. Connection for Standard Use

2.1 Connection for standard use

■ To use the TUNS1200 series, external components should be connected as shown in Fig.2.1. ■ The TUNS1200 series should be conduction-cooled. Use a heatsink or fan to dissipate heat.

Fig.2.1 Connection for standard use

Applications Manual

TUNS1200



Table 2.1 Components list

No Symbol		Item		Item Vin = 85~264VAC		Vin = 85~305VAC		Note							
nv.	0,000		1.00		Rating	Part name	Rating	Part name	NOCO						
	F 44					0325025	AOE00\//2EA	0505025							
1	F11				AC250V/25A	(littelfuse)	AC500V/25A	(Littelfuse)							
-	Input fu		Input fuse			0325025		0505025	For modical standard						
2	F12				AC250V/25A	(Littelfuse)	AC500V/25A	(Littelfuce)	application						
-					AC2101//1 EUE		AC210\//1 E.JE								
3	C11	Input cap	pacitor		ACSIUV/1.5UF	LEISS-MA × Zparallel	ACSIUV/1.5UF								
					×2parallel	(OKAYA ELECTRIC INDUSTRIES)	×2parallel	(OKAYA ELECTRIC INDUSTRIES)	_						
4	CY1	Y capacit	tor		AC400V	CD45-E2GA222M	AC400V	CD45-E2GA222M							
					/2200pF	(TDK)	/2200pF	(TDK)	_						
5	1.11				0.8mH/20A	SCR25-200-1R7A008JH	2 /mH/15A	SCR25B-150-1R4A024J							
	E11		AC Line		0.01111920A	(TOKIN)	2.41111/13A	(TOKIN)							
	1.10		filter			SC15-E350H	2 / mal 1/1E A	SCR25B-150-1R4A024J							
•	LIZ				3.3MH/13A	(TOKIN)	2.4mHy 15A	(TOKIN)							
-						LE155-MX		LE155-MX							
'	GX1				AC3IUV/1.5uF	(OKAYA ELECTRIC INDUSTRIES)	AC3IUV/I.5uF	(OKAYA ELECTRIC INDUSTRIES)							
		1	X capacitor			I E155-MX		L F155-MX	-						
8	CX2	Noico			AC310V/1.5uF	(OKAVA ELECTRIC INDUSTRIES)	AC310V/1.5uF	(OKAYA ELECTRIC INDUSTRIES)							
		filter				CD/5-E2GA152M		CD/5_F2GA152M							
9	CY2				AC400V/1500pF		AC400V/1500pF								
						CD/5 E2GA152M	-	CD/5 E2GA152M	+						
10	CY3		Y capacitor		AC400V/1500pF		AC400V/1500pF								
<u> </u>		-			AC200\//10000~F	CE/E E2CA102M v2 nemeliel	AC200\//10000		+						
11	CY4					CS45-F2GAIU3M ×2 parallel		CS45-F2GAIU3M ×2 parallel	For TUNS1200F65 only						
		-			×2parallel	(IDK)	×2parallel	(IDK)	-						
12	L3		Ferrite Bea	d	-	K5B I 4x2x2 ×2series	-	K5B I 4x2x2 ×2series	For TUNS1200F65 only						
												(King Core Electronics)		(King Core Electronics)	
			F		DC25V/2200uE	ELXZ250ELL222	DC25V/2200uE	ELXZ250ELL222							
					50201/22004	(Nippon Chemi-Con)	20201/22004	(Nippon Chemi-Con)							
			F	F28 DC50V/10	DC50V/1000uF	ELXZ500ELL102	DC50V/1000uE	ELXZ500ELL102							
13	Co	Output	out		2000 1 / 1000 al	(Nippon Chemi-Con)	2000 V/ 100001	(Nippon Chemi-Con)							
		capacito	r c		DC43\///70uE	ELXZ630ELL471	DC43\///70uE	ELXZ630ELL471							
				F48		40	DC03V/4/001	(Nippon Chemi-Con)	DC03V/4/001	(Nippon Chemi-Con)					
			E4		DC100V/150uF	UPM2A151MHD × 2parallel	DC100V/150uF	UPM2A151MHD × 2parallel							
			10		×2parallel	(Nichicon)	×2parallel	(Nichicon)							
			F12			C3216X7R1HI05		C3216X7R1H105							
					DCOUV/IUF	(TDK)	DC30V/IUF	ПТОК							
						C3216X7R1H105		C3216X7R1H105							
		Bynass	F28	28	DC50V/luF	(трк)	DC50V/IuF	πтю							
14	C40	capacitor	or	itor	apacitor			C3216X7B2A105		C3216X7R2A105	_				
			F48 F65		DC100V/1uF		DC100V/1uF								
								C3216X7B2A105		C3216X7P2A105	-				
1					DC100V/1uF		DC100V/1uF		1						
		Smoth				FLXS451VSN471 x 3parallel	DC500V///70uF	FLXS501VSN/471 x 3parallal	1						
15	15 Cbc		capacitor		x3narallel	(Ninnon Chemi-Con)	x3narallel	(Ninnon Chemi_Con)	1						
		Conacitor				FCWEE2WI05 IA x 2narallel		FCWEE2 1105 IA x 2narallal							
16	16 C20		for boost voltage		Lapacitor		apacitor or hoost voltage		apaulor for boost voltage		v2parallol	(Panasonic Electronic Componente)	x2parallol	(Panasonic Electronic Componente)	
	17 C30	Capacitor							+						
17					UC4JUV/I.UUF		UC03UV/I.UUF	CovrezJIUSJA × Zparallel							
┣──			voltage ×2pa	*zparallel	(Panasonic Electronic Components)	*∠parallel	AFMO FPI II (2 and a components)								
18	TFR1	Inrush current		5.1Ω×2series		5.1Ω×2series									
—		protectio	UNT COISTOP		(2) 2	(Ucninashi Estec)	101.0	(Ucnihashi Estec)	+						
19	R1	Discharg	jing		68k()	UR532 683	68kΩ	UR532 683	1						
		resistor		esistor ×3series x 2	×3series x 2parallel	(HOKURIKU ELECTRIC INDUSTRY)	×3series x 2parallel	(HOKURIKU ELECTRIC INDUSTRY)	_						
20	SK11 SK21	Varistor			620V	TND14V-621K	620V	TND14V-621K	1						
	SK22		0200		(Nippon Chemi-Con)			(Nippon Chemi-Con)							
21	SA11	Surne at	hsorher		4kV	DSA-402MA	4kV	DSA-402MA							
		Surgeral				(Mitsubishi Materials)	T I I	(Mitsubishi Materials)							

• External parts should be changed according to the ambient temperature, and input and output conditions.

For details, refer to the selection method of individual parts.



2.2 Input fuse: F11,F12

■ Fuse is not build-in on input side. In order to protect the unit, install a fuse (as shown in Table 2.2)

■When applying for the medical electrical equipment standard, please install F11 and F12.

Table 2.2 Recommended fuse

Input voltage range	Rated Voltage	Rated current
85 ~264VAC	AC250V以上	25A
85 ~305VAC	AC300V以上	25A

2.3 Input capacitor: C11

- ■Install a film capacitor of 3µF or higher as input capacitor C11.
- ■Use a safety approved capacitor.
- If C11 is not connected, that may cause failure of the power supply or external components.
- ■When selecting a capacitor, check the maximum allowable ripple current.
- Ripple current includes low frequency component (input frequency) and high frequency component (100kHz).
- Ripple current values flowing into C11 as listed in Table 2.1 are shown in Fig.2.2.
- The ripple current changes with PCB patterns, external parts, ambient temperature, etc. Check the actual ripple current value flowing through C11.





2.4 Y Capacitors and noise filters: CY, CX, L11, L12

- The TUNS1200 doesn't have noise filter internally
- Install an external noise filter and capacitor (CY) to reduce conducted noise and stabilize the operation of the power supply.
- Noise filters should be properly designed when the unit must conform to the EMI/EMS standards or when surge voltage may be applied to the unit.
- Install the primary Y capacitor (CY1) as close as possible to the input pins (within 50 mm from the pins).

A capacitance of 470 pF or more is required.

- When the total capacitance of CYs exceeds 8,800 pF, input-output withstanding voltage may be dropped. In this case, either reduce the capacitance of Y capacitors or install a grounding capacitor between output and FG.
- Use capacitors that comply with safety standards as CY.

2.5 Output capacitors: Co, C40

■ Install an external capacitor, Co, between +VOUT and -VOUT pins for stable operation of the power supply. Recommended capacitance of Co is shown in Table 2.3.

Use low impedance electrolytic capacitors with excellent temperature characteristics.
 When Using at ambient temperatures below 0 °C, the output ripple voltage increases due to the characteristics of equivalent series resistor (ESR). In this case, connect three capacitors, Co, of recommended capacitance in parallel connection.

■Specifications, output ripple and ripple noise as evaluation data values are measured according to Fig.2.3.

Table 2.3 Recommended capacitance Co

2.3	Output Voltage	$Tc = 0 \sim 100^{\circ}C$	$Tc = -40 \sim 100^{\circ}C$
ded	12V	2,200uF	2,200uF×3parallel
ince	28V	1,000uF	1,000uF×3parallel
Co	48V	470uF	470uF×3parallel
	65V	150uF×2parallel	150uF×6parallel

Fig.2.3 Measuring environment



2.6 Smoothing capacitor for boost voltage: Cbc

■ In order to smooth boost voltage, connect Cbc between +BC and -BC.

- Recommended capacitance of Cbc is shown in Table 2.4.
- If the capacity is not within the allowable external capacity, the module may be damaged.
- When operated below 0°C, operation may become unstable as boost ripple voltage increases due to ESR characteristics. Choose a capacitor which has higher capacitance than recommended.

Select a capacitor so that the ripple voltage of the boost voltage is 30 Vp-p or below.

- If the ripple voltage of the boost voltage increases, the ripple current rating of the smoothing capacitor may be exceeded. Check the maximum allowable ripple current of the capacitor.
- The ripple current changes with PCB patterns, external parts, ambient temperature, etc. Check the actual ripple current value flowing through Cbc.
- The boost voltage varies depending on the input voltage. (See item 3.1)

Table 2.4 Recommended capacitance Cbc

Input voltage range	Rated voltage	Rated voltage Recommended Allowak capacitor capacitance	
85 ~264VAC	DC420V以上	470uF×3 parallel	780uF ~ 3,300uF
85 ~ 305VAC	DC500V以上	470uF×3 parallel	780uF ~ 2,200uF

 \times Refer to item 3 and 4 for selection method of Cbc.



*Ripple current value is the sum of parallel capacitors.



2.7 Capacitor for boost voltage :C20,C30

■Install a film capacitor of 2uF or more into C20 and C30.

- If C20 and C30 are not connected, the power supply or external components could be damaged.
- Ripple current flows in. Check the maximum allowable ripple current of the capacitor when selecting. The frequency of the ripple current is 100 kHz to 200 kHz.
- Ripple current values flowing into C20 and C30 as listed in Table 2.1 are shown in Fig.2.5 and Fig.2.6.
- The ripple current changes with PCB patterns, external parts, ambient temperature, etc. Check the actual ripple current values flowing through C20 and C30.

The boost voltage varies depending on the input voltage. (See item 3.1)



*Ripple current value is the sum of parallel capacitor



%Ripple current value is the sum of parallel capacitor

2.8 Inrush current limiting resistor: TFR1

■Install inrush current limiting resistor (TFR1) between R terminal and +BC terminal.

- If TFR1 is not connected, the power supply will not work.
- The surge capacity is required for TFR1.
- ■Wirewound resistor with thermal cut-offs type is required.
- Inrush current limiting resistor can be used to limit the primary inrush current. However, the secondary inrush current can't be limited by increasing the resistor value of inrush current limiting resistor. The secondary inrush current is approx. 25 ~ 30A. Therefore, we don't recommend connecting a large resistance as TFR1.
- The inrush current changes by PCB pattern, parts characteristic etc.
 Check the actual inrush current value flowing through the AC line.

Table 2.5 Recommended resistor TFR1

Recommended resistance	
$4.7\Omega \sim 22\Omega$	

- The selection method of TFR1 is shown below.
- Calculation of resistance

Resistance can be calculated using the following formula.

$$TFR1 = \frac{Vin \times \sqrt{2}}{Ip} - R_L[\Omega]$$

TFR1 : Inrush current limiting resistor

- RL : Line impedance
- Vin : Input voltage (rms)
- Ip : Primary Inrush current (peak)

• Calculation of required surge capacity Required surge capacity can be calculated using the following formula. Please contact to the component manufacturer regarding the surge current withstanding capability.

$$I^{2}t = \frac{Cbc \times Vin^{2}}{TFR1}[A^{2}s]$$

I2t : Current squared times

- TFR1 : Inrush current limiting resistor
 - Cbc : Smoothing capacitor for boost voltage
 - Vin : Input voltage (rms)

2.9 Discharging resistor: R1

- If you need to meet the safety standards, install a discharging resistor R1 at input interphase capacitors.
- Please select a resistor so that the input interphase voltage decreases in 42.4V or less at 1 second after turn off the input.
- Fig.2.7 shows the relationship between a necessary resistance of R1 and total capacitance of input interphase capacitors. The data is the value assuming the worst condition.
 Please keep margin for rated voltage and power of R1.

Fig.2.7 Relationship between input interphase capacitors and discharging resistor R1.





3.1 Input voltage characteristics of boosted voltage





3.2 Holdup time

■ Holdup time is determined by the capacitance of Cbc. Figure 3.2 shows the relationship between holdup time and output current.



4. Operation Under Low Temperature Conditions

4.1 Ripple voltage of boost voltage

Applications Manual

TUNS1200

- ■At low temperature, ripple voltage of boost voltage increases due to Cbc freezes. Select a capacitor of which ripple voltage of boost voltage does not exceed 30Vp-p on an actual operating condition.
- And check the maximum allowable ripple current of the capacitor.
- Fig.4.1,4.2 shows the relationship between ripple voltage of BC and temperature.







5. Parallel operation

Applications Manual

TUNS1200

5.1 Wiring for parallel operation

■ Parallel operation is available by connecting the units as shown in Fig 5.1.

- Input capacitor C11, boost voltage circuit capacitor (Cbc, C20, C30) and Inrush current limiting resistor TFR1 cannot be used together. Please wire for each power supply .
- Total current should not exceed the value calculated by the following equation, and total number of unit should be no more than 9 pieces.

(Output current at parallel operation) = (the rated current per unit)× (number of unit) ×0.9

- Connect the sensing line and the power line by one point after connecting each power supply's sensing pin(+S,-S). Please do not connect the sensing from the individual power supply as it may cause unstable operation.
- Please make sure that the wiring impedance of a load from each power supply become even.
- Output voltage and constant current can be adjusted in parallel operation. (Refer to item 5.2, 5.3)
- When the input voltage is applied with remaining the voltage at boost capacitor Cbc, startup time would be different for each paralleled module. If all paralleled modules need to startup at the same time, remote control function shall be used.
- If the output current is less than 2% of the rated current, the output voltage ripple will be large. Therefore, it is recommended to use it with 2% load or more.





5.2 Output voltage adjustment in parallel operation(CV)

- When adjusting the output voltage in parallel operation, connect the VTRM terminals together and adjust them together.
- ■By connecting the external potentiometer (VR1) as shown in Fig.5.2.,output voltage becomes adjustable. See formula①



■ By connecting the external power supply as shown in Fig.5.3.,output voltage becomes adjustable.





5.3 Constant current adjustment in parallel operation(CC)

By adjusting the voltage of one ITRM, it is possible to adjust the constant current of all power supplies connected in parallel. It is not necessary to connect all ITRM terminals.
 By connecting the external potentiometer (VR2) as shown in Fig.5.4.,constant current becomes adjustable. See formula⁽²⁾



■ By connecting the external power supply as shown in Fig.5.5.,constant current becomes adjustable.



5.4 N+1 redundant operation

■If you add one extra power supply in parallel operation, even if one of the power supplies in your system fails, the remaining power supplies continue to function.

■Use the load current with N power supplies, and keep the current per unit below the rated current x 0.9 or less.

Constant current control cannot be used in N+1 redundant operation.

- ■The remote sensing function cannot be used in N+1 redundant operation.
- At the load end, the voltage drops due to the forward voltage (Vf) of the diode
- ■If there is a difference in the timing of input voltage application between redundantly connected modules (For example, if input voltage is applied to one module and it starts up, and then input voltage is applied to another module), all modules will stop once and then start up. To start up the modules without stopping, an external circuit is required separately. Please contact us for more information on external circuit.
- ■When the output voltage is adjusted by the volume in N+1 redundant operation, connect the volume to each power supply as shown in Fig.5.6.





■ By connecting the external power supply as shown in Fig.5.7.,output voltage becomes adjustable.





5.5 Remote control

■ When using remote control in parallel operation, control the remote control terminals of the power supplies in parallel at the same time, as shown in Fig.5.8 and 5.9.

Ex.1) When the power output terminal and the remote control circuit are not isolated

Fig.5.8. Remote control wiring example



 \therefore In the case of this connection example, the control current (I_RC1) flows up to 9.7mA. Current (N×I_RC1) for parallel connection (N) flows to the control switch.

Control current(I_RC1) = 9.7mA

••••①



When determining Vrc and Rrc, the current (I_RC1) flowing through each remote control circuit must satisfy the following formulas (2) and (3).
 Current (N×I_RC1) for parallel connection (N) flows to the control switch.

6. Other functions

6.1 Power Good

Applications Manual

TUNS1200

By using PG, it is possible to monitor power supply whether normal operation or abnormal operation. The PG signal is "Low" when the power supply operates correctly. The signal turns to "High" when the power supply stops.
 The PG signal sequence is shown in Fig6.1.



 $\times 1$ V1 :60% of the set output voltage

 $\ensuremath{\overset{\scriptstyle\bullet}{\times}} 2\ \ensuremath{\,\mathrm{V2}}\ : 20\%$ of the rated output voltage



6.2 Output Current Monitor

- The output current can be monitored by voltage between the CB and -S.
- Fig.10.1 shows the relationship between the voltage of CB terminal and the output current. The output current shown in Fig.10.1 is for reference only.
- Output current monitor circuit example shown in Fig.10.2.



Please note the following when using the output current monitor.

- \blacksquare Use a measuring instrument whose input impedance is 500k Ω or more.
- Do not connect more than 0.01µF to CB terminal to prevent output voltage malfunction.
- Wire carefully to avoid malfunction caused by noise.
- The pulse load cannot be monitored.

7. Mounting method

Applications Manual

TUNS1200

7.1 Mounting method

When implementing the power supply to the printed circuit board, please fix the power supply to the printed circuit board by screw before the soldering.

If it is screwed to the substrate after soldering, there is a possibility of failure by adding mechanical stress to the soldering point and the internal connections of power supply.



8. Board layout

Applications Manual

TUNS1200



+BC -BC

R

4-FG



- When installing the electrolytic capacitor and the power supply on the same surface of the printed circuit board, please pay attention to the distance between the base plate and electrolytic capacitor. Exterior of the electrolytic capacitor is assumed to be the same potential as the negative electrode.
- High-frequency noise radiates directly from the unit to the atmosphere. Therefore, design the shield pattern on the printed circuit board and connect to FG. The shield pattern prevents noise radiation.



There are notes for printed circuit board design at recommended circuit in this applications manual. Please see below.



1 Input fuse : F11

When the fuse is blown out, input voltage would be applied between the terminals of the fuse F11.

Please keep the distance of the pattern between the terminals of the fuse more than 3mm if you must be complied safety approvals.



Noise filter is build by Line filters (L11, L12), X capacitor (CX1, CX2) and Y capacitor (CY2,CY3). And the Noise filter is used to reduce conduction noise from power supply. Off-the-shelf Noise filter is also available.

If the Line filter is placed near the components which is switching at high frequency, the conduction noise may be increased because the noise goes into the Line filter. Therefore, the Line filter should be shielded or keep the distance from the source of noise.



The effect of noise reduction by Y capacitor depends on the place of the FG connection. Recommend connecting Y capacitor to the FG terminal of the power supply as close as possible. Please evaluate before use.

③ Input capacitor : C11

Huge ripple current flows into the capacitor C11. Place the capacitor C11 near the power supply as close as possible.

(4) Inrush current limiting resistor : TFR1

Inrush current will flow through the Cbc TRF1 from the R pin. Please have a pattern width that is not damaged by the inrush current.

 ⑤ Capacitor for boost voltage : Cbc,C20 R pin connected capacitor : C30
 The high voltage is appeared between +BC,R and -BC terminals. The distance between +BC, R and -BC terminals must be 3mm or more. Huge ripple current flows into the capacitor C20. Place C20 near the power supply as close as possible.
 ⑥ Y Capacitors : CY1

CY1 should be connected to the FG terminal of the power supply as close as possible.

⑦ Output capacitors : Co, C40

Connecting the output capacitor (Co,C40) to the power module as close as possible for stable operation and radiation noise reduction.

The output line impedance could cause unstable output voltage, which can be reduced by adding the output capacitor close to the load.

When the output ripple and ripple noise must be reduced, ceramic capacitor C40 which has good characteristics at high frequency should be used.

If through-hole type ceramic capacitor is used, the effect of the noise reduction would be reduced by the impedance of the lead frame of the components.

Please evaluate before using.

8 FG terminals of the power supply

Connect the FG terminal of the power supply to the PWB by screw. If the FG terminals of the power supply is not connected properly, malfunction or failure could happen. Expose the solder mask around the hole of the FG connection on the PWB to connect FG terminals by screws.

9 Surge Suppression Device: SK11,SK21,SK22, and SA11

In isolation test, test voltage is applied to the SA11. When the test voltage beyond the specification of the SA11 is applied, please remove the SA11 during the test, or lower the test voltage.

Note. When conducting isolation test between the primary and the secondary, high voltage is applied to SA11,SK11,SK21, and SK22, by the partial pressure of the Y capacitor.

1 Discharging resistor : R1

Please keep distance between electrodes, when using multiple resistors as R1 due to the power loss dispersion.

In the case of obtaining safety standards, please keep insulation distance required by the standards.





① Secondary Y capacitor : CY4

Since the output voltage of TUNS1200F65 exceeds the safe voltage (60V), basic insulation is required between the secondary and FG. Y capacitors CY4 must be Y2 class safety standard certified.

CY4 should be connected to the FG terminal of the power supply as close as possible.



8.2 Reference PCB layout



PCB size: 150 x 362.5mm PCB thickness: 1.6mm copper thickness: 35um

(a) Example of the pattern and components layout (Top layer)



(b) Example of the pattern and components layout (Bottom layer)



9. Thermal Design

Applications Manual

TUNS1200

9.1 Thermal Design

Please refer to the applications manual "9.Thermal Considerations" on our website.

https://en.cosel.co.jp/technical/app_guide/module_type/pdf/thermal_considerations.pdf

9.2 Examples of Convection cooling

Here is an example of convection cooling with heatsink.

■ Please consider this example as a design guideline because it changes by the heat dissipation environment. Please measure the temperature of the actual equipment eventually.





*Measurement results with TUNS1200F28

9.3 Examples of Forced air cooling

Applications Manual

TUNS1200

- Here is an example of forced air cooling with heatsink.
- Please consider this example as a design guideline because it changes by the heat dissipation environment. Please measure the temperature of the actual equipment eventually.
- If it is difficult to measure the center of the baseplate, please measure the leeward side of the baseplate edge.







*Measurement results with TUNS1200F28

Revision history

Applications Manual

TUNS1200

No.	date	Rev.	page	content
1	2021.11.22	1.1E	A-23 ~ A-25	「9 Thermal Design」Addition
2	2022.6.20	1.2E	A-2,A-4 A-20,A-22	External parts for TUNS1200F65 Addition
3	2022.6.20	1.2E	A-16	「6.2 Output current monitor」Addition
4	2022.6.20	1.2E	A-13	「5.3 Constant current adjustment in parallel operation(CC)」 Recommended Circuit Change (Fig.5.4 ,5.5)
5	2022.6.20	1.2E	A-14	Note on N+1 redundant operation Addition
6				
7				
8				
9				
10				
11				
12				
13				
14				
15				
16				
17				
18				
19				
20				